

Power supply project

Student: Pop Razvan Valentin

Contents


Transformer	3
Rectifier	4
Linear regulator with transistor	8
Power supply project – Voltage regulator with integrated circuit	10
Buck Converter Step Down	13
The PID controller	18

Transformer


1.Description

A power supply is an electrical device that supplies electric power to an electrical load. The primary function of a power supply is to convert electric current from a source to the correct voltage, current, and frequency to power the load.

2.Components of power supply

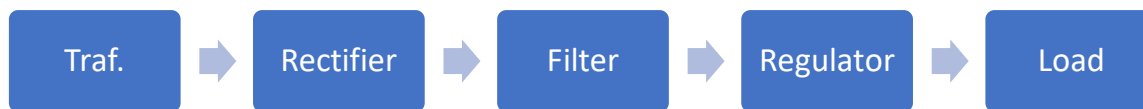

3.The transformer

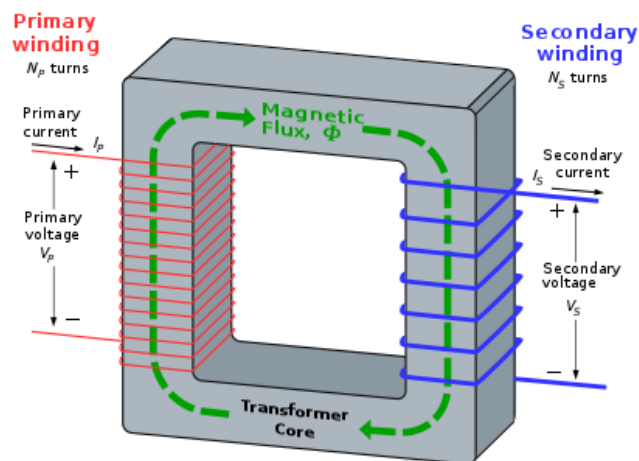

A transformer is a passive component that transfers electrical energy from one electrical circuit to another circuit, or multiple circuits. A varying current in any one coil of the transformer produces a varying magnetic flux in the transformer's core, which induces a varying electromotive force across any other coils wound around the same core.

4.Selecting a transformer for our need

Our transformer needs to be able to power the following: a transistor regulator with the specs: 12V 0.5A efficiency 30%, I.C Regulator with the specs: 5V 1A efficiency 30% and a Buck Converter with the specs: 3.3V 4A and efficiency 90%.

It has to work with the following input : 230 VAC and rated frequency of 50-60Hz

We compute the power needed for each input component as follows:

$$n = \frac{P_{out}}{P_{in}}$$

$$P_{in} = \frac{I \times V}{n}$$


1. Input power for the transistor regulator is 20W
2. Input power for the I.C regulator 16.6 W
3. Input power for the buck : 14.66w
4. Total of power needed : 51.32 W

U1 = 230V

U2 = 18 V

I_{max} = 4A

Chosen transformer **58-0100-018-S:**

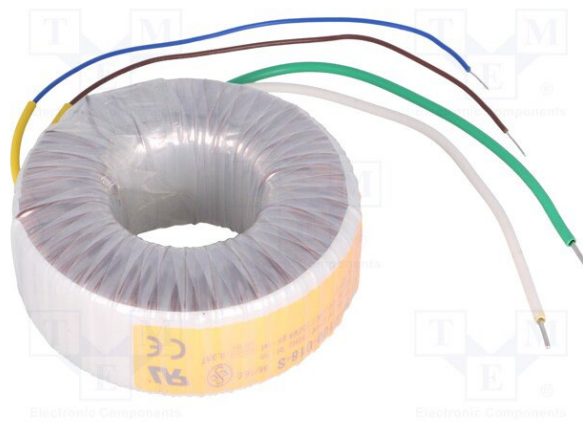

Rectifier

1.Type and circuit of rectifier used

Full-wave rectifier with capacitive filter and simulation of the circuit before any values for this project.

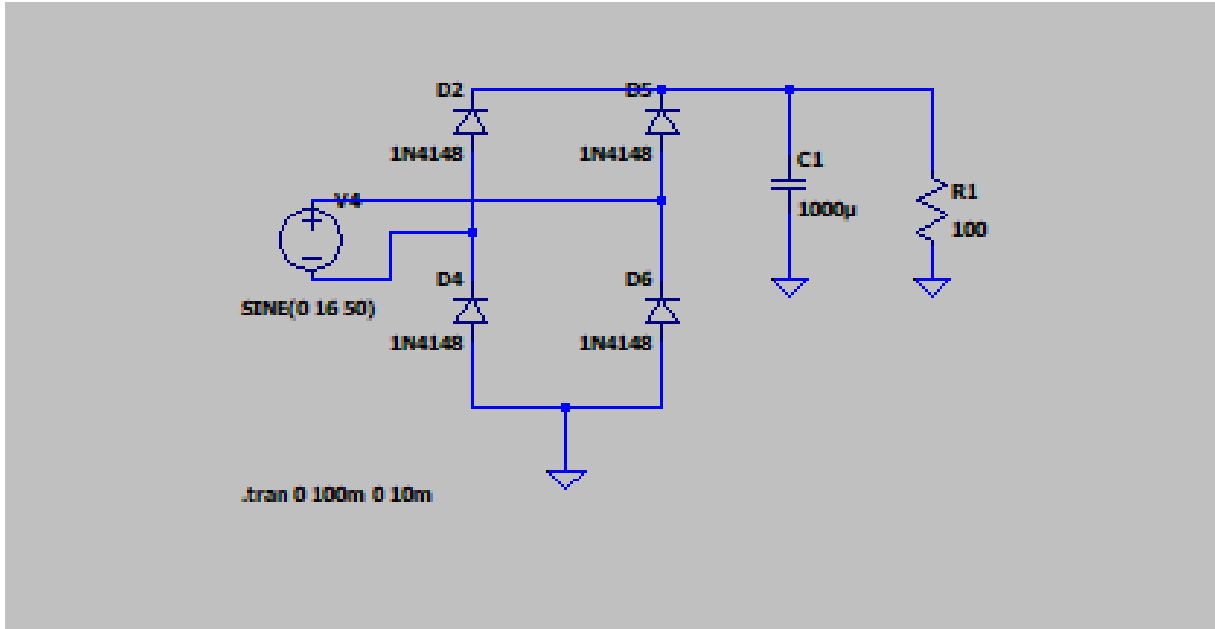


Figure 1 Circuit of full-wave rectifier with capacitive filter

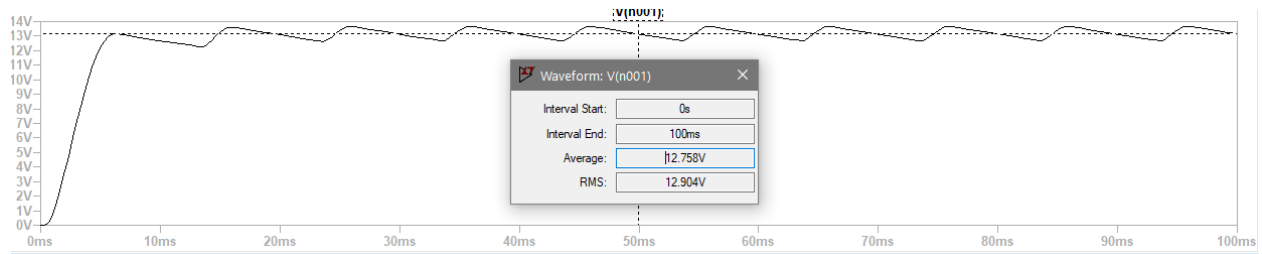


Figure 2 Output of the circuit with 16v input and 1N4148

2.Configuration

$$V_{out_{rectifier}} = 16V$$

$$P_{out_{rectifier}} = 51.32W$$

$$\eta \geq 70\%$$

$$\Delta V_{out} = 0.5 V$$

$$f_{in} = 50Hz$$

3.Computations

$$I_{out} = \frac{P_{out_{rect}}}{V_{out_{rect}}} = 3.2 A$$

$$\gamma = \frac{\frac{\Delta V_{out}}{2}}{V_{out_{rectifier}}} = 0.016 - ripple\ factor$$

$$f_{out} = 2 * f_{in} = 100 Hz$$

$$\omega = 2 * \pi * f_{out} = 628.31 \frac{rad}{s}$$

$$R_s = \frac{V_{out_{rectifier}}}{I_{out_{rectifier}}} = 4.98 \cong 5 \text{ Ohm}$$

$$C = \frac{\pi}{2 * \omega * R_s * \gamma} = 0.032 \text{ F} = 32 \text{ mF}$$

$$V_{in_{rect}} = V_{out} + 2 * V_F \cong 18 = V_{D_{max}}$$


VF considered 0.8

$$I_{D \text{ max}} = \sqrt{(\pi * \omega * R_s)} * I_{out_{rectifier}} = 57 \text{ A}$$

4.Result from calculation

We need a diode that can support at least 57 A and 18 V.

The diode chosen :

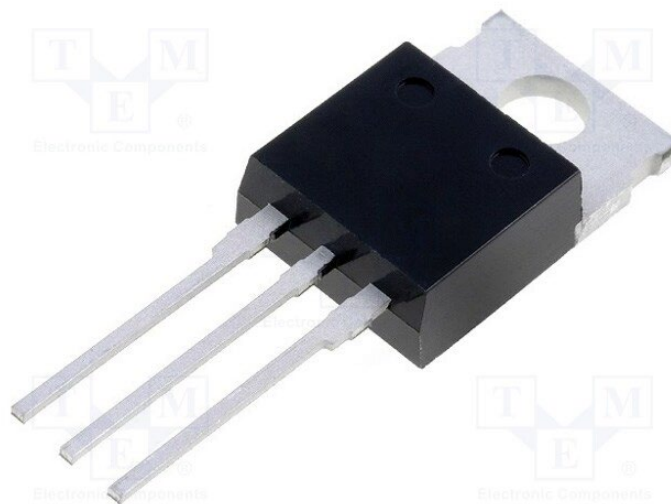

Manufacturer	ONSEMI
Type of diode	Schottky rectifying
Mounting	THT
Max. off-state voltage	100V
Load current	2x 30A
Max. load current	60A
Semiconductor structure	common <u>cathode_double</u>
Case	TO220-3
Kind of package	tube
Heatsink thickness	1.15...1.39mm
Max. forward impulse current	350A
Max. forward voltage	0.81V

5. Simulations with the results and a similar Schottky diode

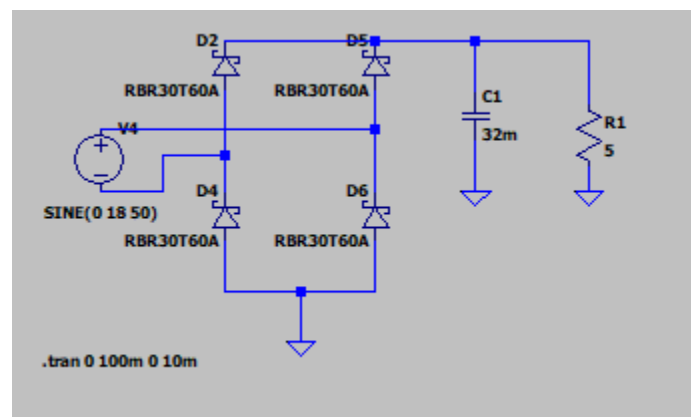


Figure 3 New circuit with changed values accordingly


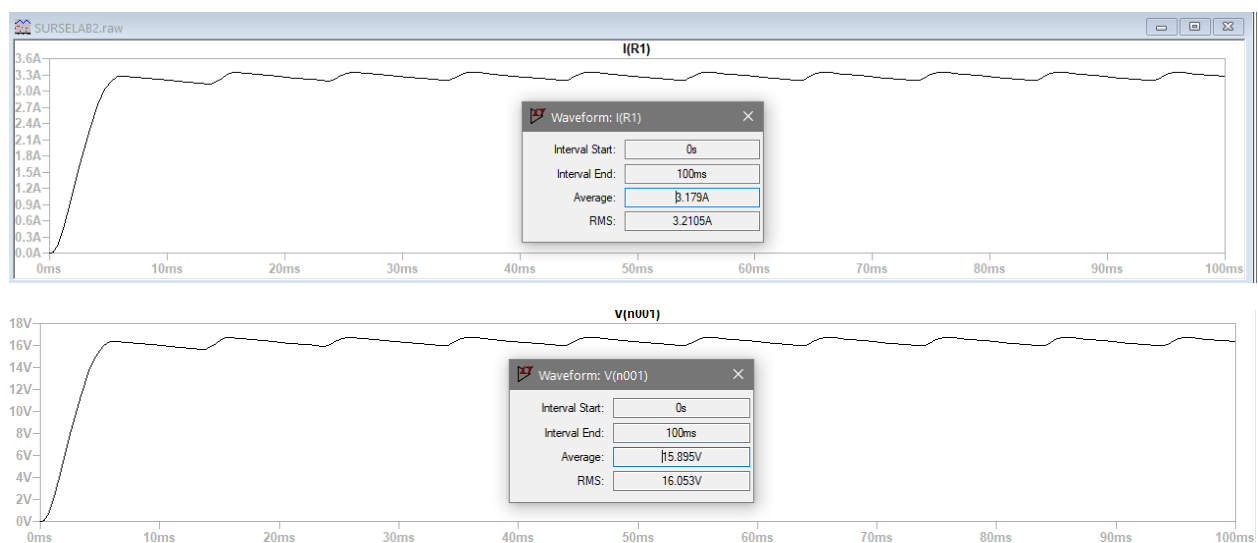



Figure 4 Results of simulation

Linear regulator with transistor

Circuit:

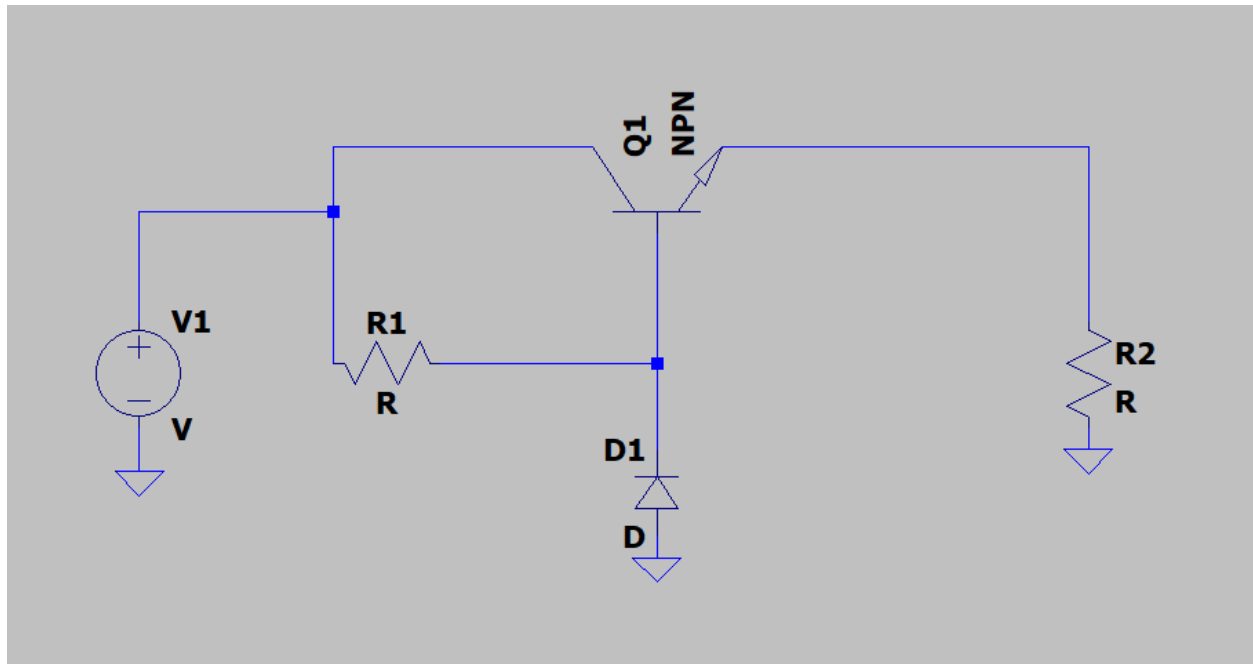

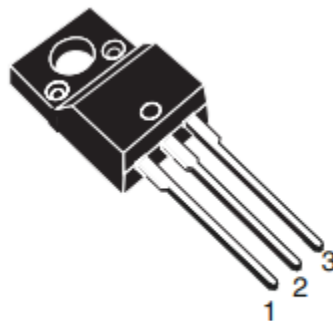Choosing a transistor **2STP535FP** with high h_{FE} :



TO-220FP

h_{FE}	4000
V_{BE}	5V
Total dissipation	37W
V_{CE}	180V

Calculus :

$$\eta := 30\%$$

$$V_{in} := 16 \text{ V}$$

$$V_{in_min} := 15.8 \text{ V}$$

$$I_z := 10 \text{ mA}$$

$$\beta := 4000$$

$$V_{out} := 12 \text{ V}$$

$$V_{in_max} := 16.2 \text{ V}$$

$$I_{out} := 0.5 \text{ A}$$

$$T_a := 35 \text{ }^\circ\text{C}$$

$$V_{BE} := 5 \text{ V}$$

$$P_{out} := V_{out} \cdot I_{out} = 6 \text{ W} \quad P_{in} := \frac{P_{out}}{\eta} = 20 \text{ W}$$

$$LOAD := \frac{V_{out}}{I_{out}} = 24 \text{ } \Omega \quad I_{in} := \frac{P_{in}}{V_{in}} = 1.25 \text{ A}$$

$$I_E := I_{out} = 0.5 \text{ A} \quad I_C := I_E \quad I_B := \frac{I_{out}}{\beta + 1} = 124.969 \text{ } \mu\text{A}$$

$$I_r := I_z + I_B = 0.01 \text{ A}$$

$$V_Z := V_{out} + V_{BE} = 7 \text{ V}$$

$$P_D := P_{in} - P_{out} = 14 \text{ W}$$

$$P_Z := V_Z \cdot I_z = 0.07 \text{ W}$$

$$P_T := 13.83 \text{ W}$$

$$V_R := V_{in} - V_Z = 9 \text{ V}$$

$$R := \frac{V_R}{I_r} = 888.892 \text{ } \Omega$$

$$P_R := V_R \cdot I_r = 0.091 \text{ W}$$

Diode BZX84C7V5:




V _Z	7.45
P _Z	0.35W
I _Z	5mA

Resistance after modifying the Zener current

$$R := \frac{V_R}{I_r} = 1.756 \text{ k}\Omega$$

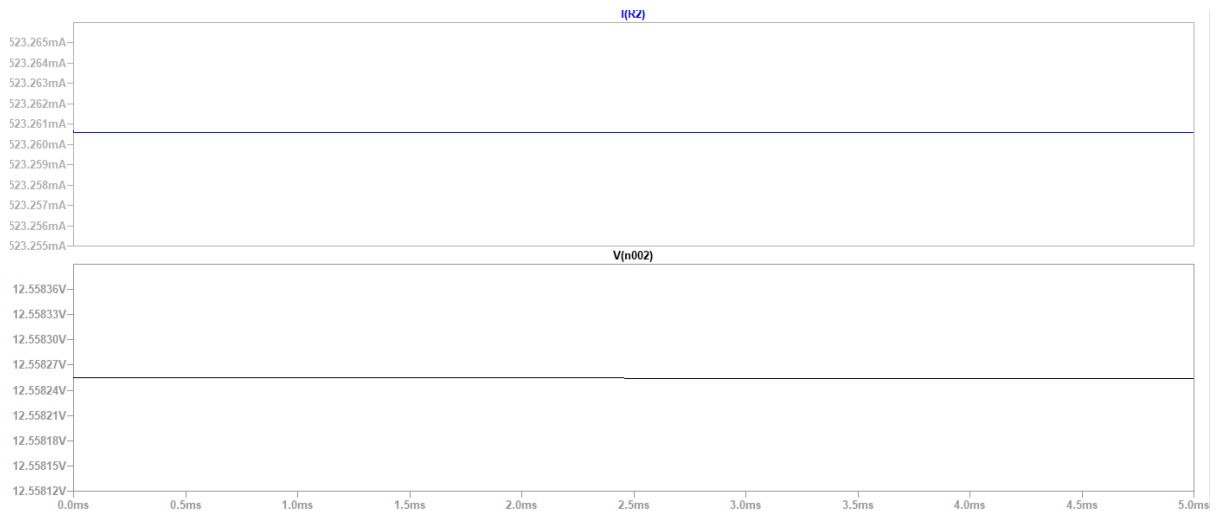Output results running a transient analysis for 5ms




Power supply project – Voltage regulator with integrated circuit



1. Voltage regulator chosen - **LM7805**



Manufacturer	TEXAS INSTRUMENTS
Voltage drop	2V
Output voltage	1.5A

2.Circuit used and simulation

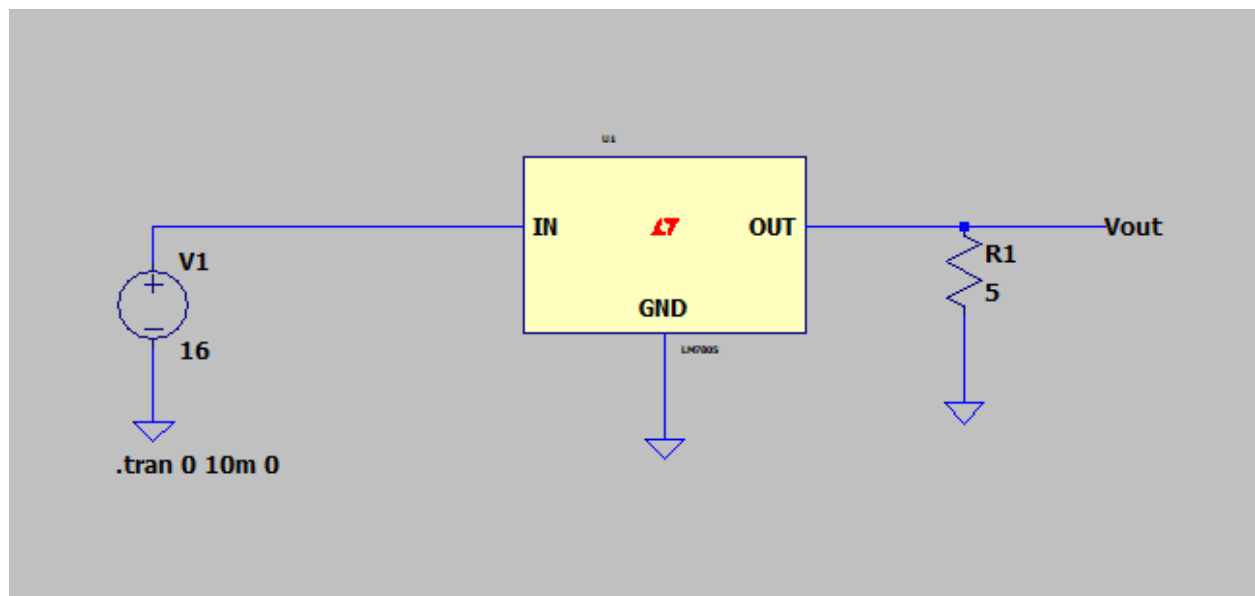

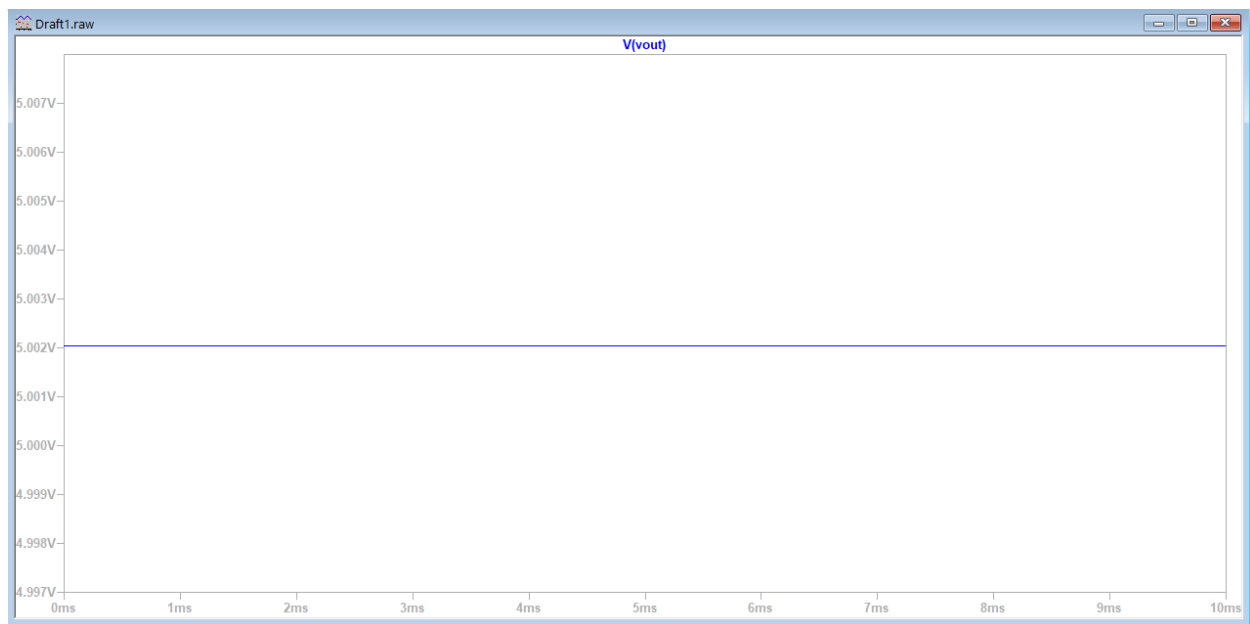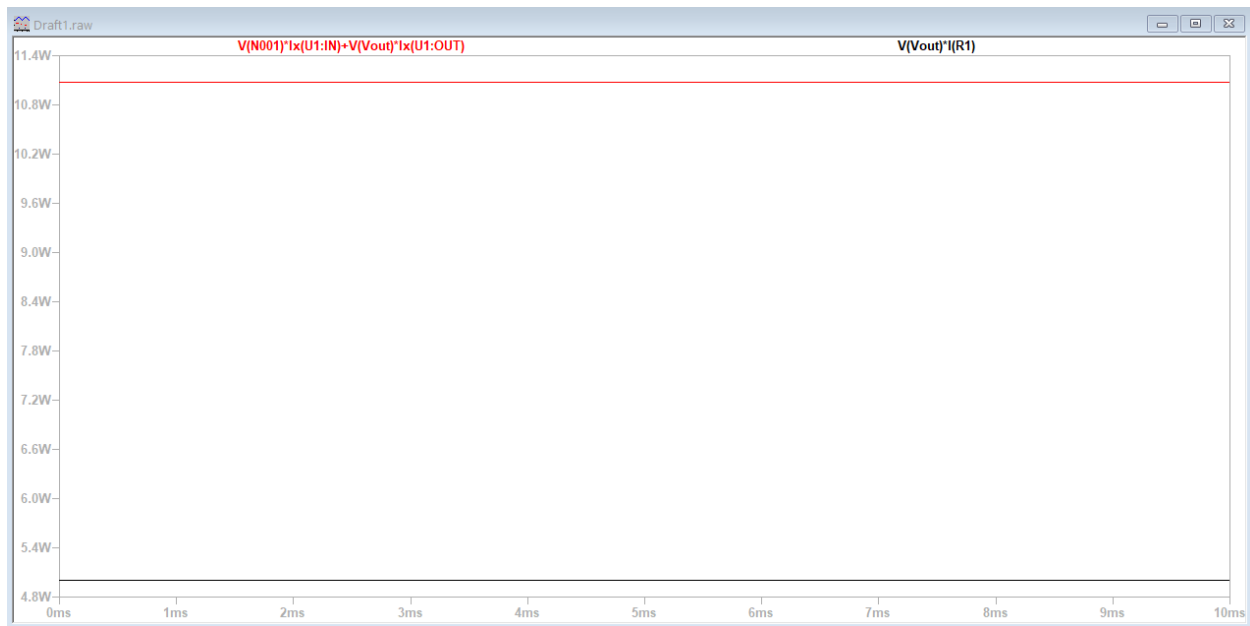


3. Load resistance calculation and choosing - 90J5R0E

$V_{in} := 16 \text{ V}$
 $V_{out} := 5 \text{ V}$
 $I_{out} := 1 \text{ A}$
 $P_{out} := V_{out} \cdot I_{out} = 5 \text{ W}$
 $n := 30$
 $P_{in} := \frac{(100 \cdot P_{out})}{n}$
 $P_{in} = 16.667 \text{ W}$
 $I_{in} := \frac{P_{in}}{V_{in}} = 1.042 \text{ A}$
 $R_{Load} := \frac{V_{out}}{I_{out}} = 5 \Omega$
 $T_{JMAX} := 125$
 $T_A := 25$
 $P_D := (V_{in} - V_{out}) \cdot I_{out} = 11 \text{ W}$
 $\theta_{JA} := 19 \frac{C}{W}$
 $\theta_{JC} := 3 \cdot \frac{1}{W} \frac{C}{W}$
 $\theta_{JATOTAL} := \frac{(T_{JMAX} - T_A)}{P_D} = 9.091 \frac{1}{W} \frac{C}{W}$
 $\theta_{SA} := \theta_{JATOTAL} - \theta_{JC} = 6.091 \frac{1}{W}$

for LM7805
 5 W resistor
 Since $\theta_{JA(TOTAL)} < \theta_{JA}$, a heat sink will definitely be required.

Buck Converter Step Down

Circuit:

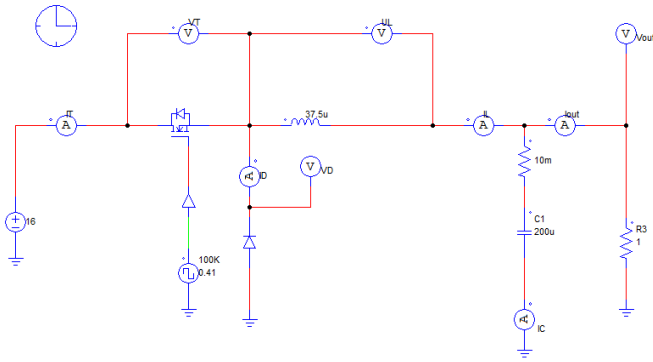

Calculations:

Specifications

$$U_{in_max} := 16 \text{ V} \quad f_c := 100 \text{ kHz} \quad I_{out_min} := 400 \text{ mA}$$

$$U_{in_min} := U_{in_max} \quad r_{pl} := 20 \text{ mV} \quad I_{out_max} := 4 \text{ A} \quad T := \frac{1}{f_c} = 10 \text{ } \mu\text{s}$$

$$U_{forward} := 0.5 \text{ V} \quad U_{ripple} := 0.2 \text{ V} \quad U_S := 3.3 \text{ V} + 0.5 \text{ V} + 0.2 \text{ V} = 4 \text{ V}$$

Output voltage due to non-ideal conditions

$$T_C := T \cdot \left(\frac{U_S}{U_{in_max}} \right) = 2.5 \text{ } \mu\text{s} \quad \delta := \frac{U_S}{U_{in_max}} = 0.25 \quad 25\% \quad T_B := T \cdot \left(1 - \frac{U_S}{U_{in_max}} \right) = 7.5 \text{ } \mu\text{s}$$

$$I_{Dmax} := I_{out_max} = 4 \text{ A} \quad I_{Dmed} := I_{out_max} \cdot (1 - \delta) = 3 \text{ A}$$

$$L_{min} := \frac{(U_S \cdot T)}{2 \cdot I_{out_min}} \cdot \left(1 - \frac{U_S}{U_{in_max}} \right) = 37.5 \text{ } \mu\text{H} \quad U_{TMAX} := U_{in_max} = 16 \text{ V}$$

$$I_{Lmin} := I_{out_max} - \frac{(U_S \cdot T)}{2 \cdot L_{min}} \cdot \left(1 - \frac{U_S}{U_{in_max}} \right) = 3.6 \text{ A} \quad I_{Lmax} := I_{out_max} + \frac{(U_S \cdot T)}{2 \cdot L_{min}} \cdot \left(1 - \frac{U_S}{U_{in_max}} \right) = 4.4 \text{ A}$$

$$I_{Lmax} := 2 \cdot I_{out_max} - I_{Lmin} = 4.4 \text{ A} \quad I_{Lmax_disc} := \frac{(U_{in_max} - U_S) \cdot T_C}{L_{min}} = 0.8 \text{ A}$$

$$U_L := L_{min} \cdot \left(\frac{(I_{Lmax} - I_{Lmin})}{T_C} \right) = 12 \text{ V} \quad \text{Maximum current discontinuous}$$

$$Q := \frac{T^2}{8} \cdot \frac{\left(1 - \frac{U_S}{U_{in_max}} \right) \cdot U_S}{L_{min}} = 1 \text{ } \mu\text{C} \quad I_{cef} := \frac{I_{out_min}}{\sqrt{3}} = 0.231 \text{ A}$$

$$C := \frac{1}{8} \cdot \frac{\left(1 - \frac{U_S}{U_{in_max}} \right) \cdot U_{in_max} \cdot T^2}{L_{min} \cdot 20 \text{ mV}} = 200 \text{ } \mu\text{F} \quad R_{load} := \frac{U_S}{I_{out_max}} = 1 \text{ } \Omega$$

Choosing the components:

Diode - Schottky SD1040CS_S2_00001



Maximum current 5A V_{rrm} - Repetitive Reverse Voltage: 40 V V_f - Forward Voltage: 550 mV

Maximum average forward rectified current – 10A

Price 5 Ron

Transistor - RQ6E050AJTCR N-CHANNEL



I_D 5A $V_{gs\ th}$ - Gate-Source Threshold Voltage: 500 mV

V_{ds} - Drain-Source Breakdown Voltage: 30 V

Price 3 Ron

Capacitor MCAX25V207K8X16



Voltage Rating: 25V

Price 4 Ron

Capacitance Tolerance: $\pm 10\%$


Inductor - PL8916NL






Inductance: 37.6 μH

Maximum DC Current: 11 A

Simulations:

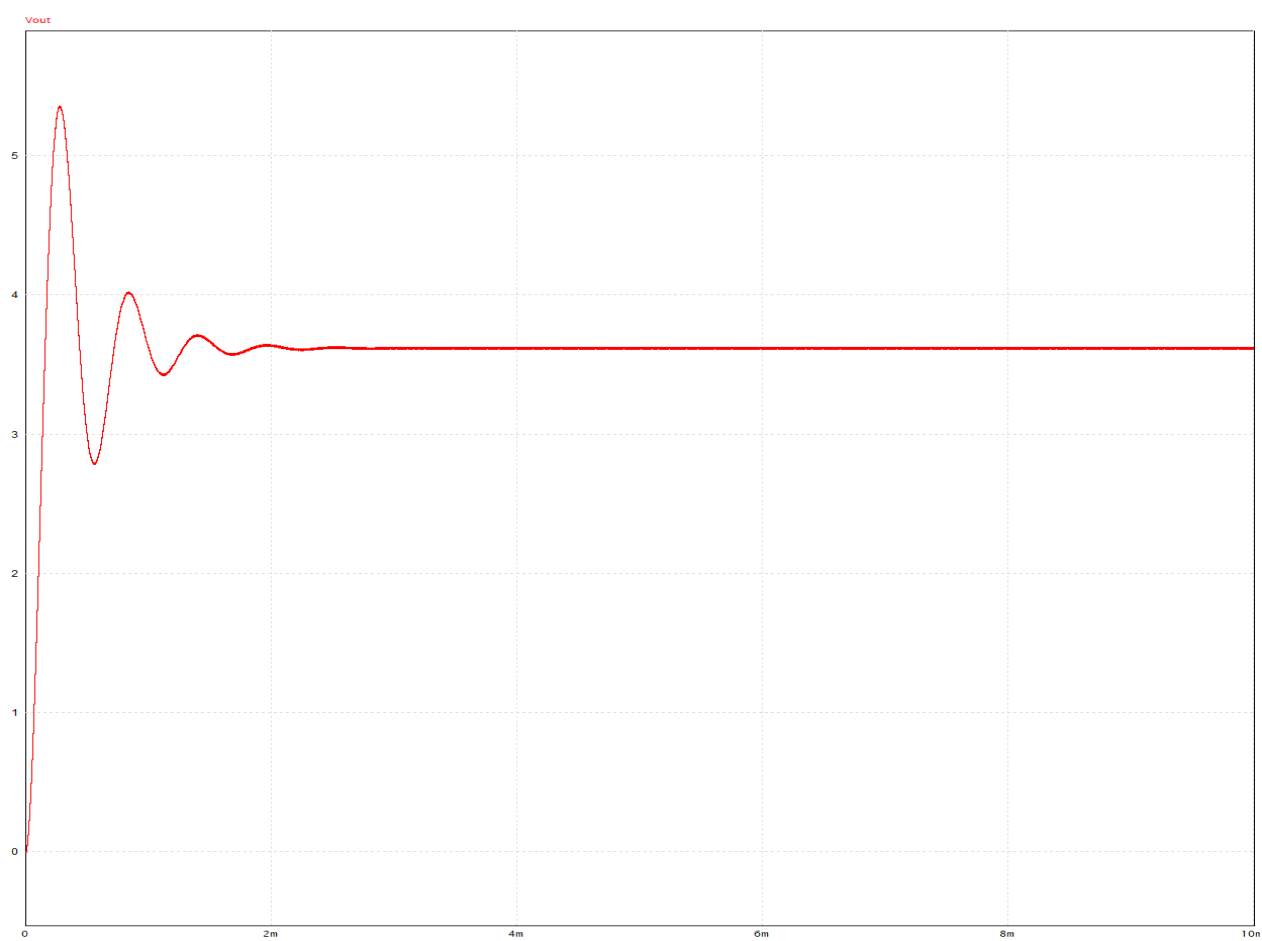

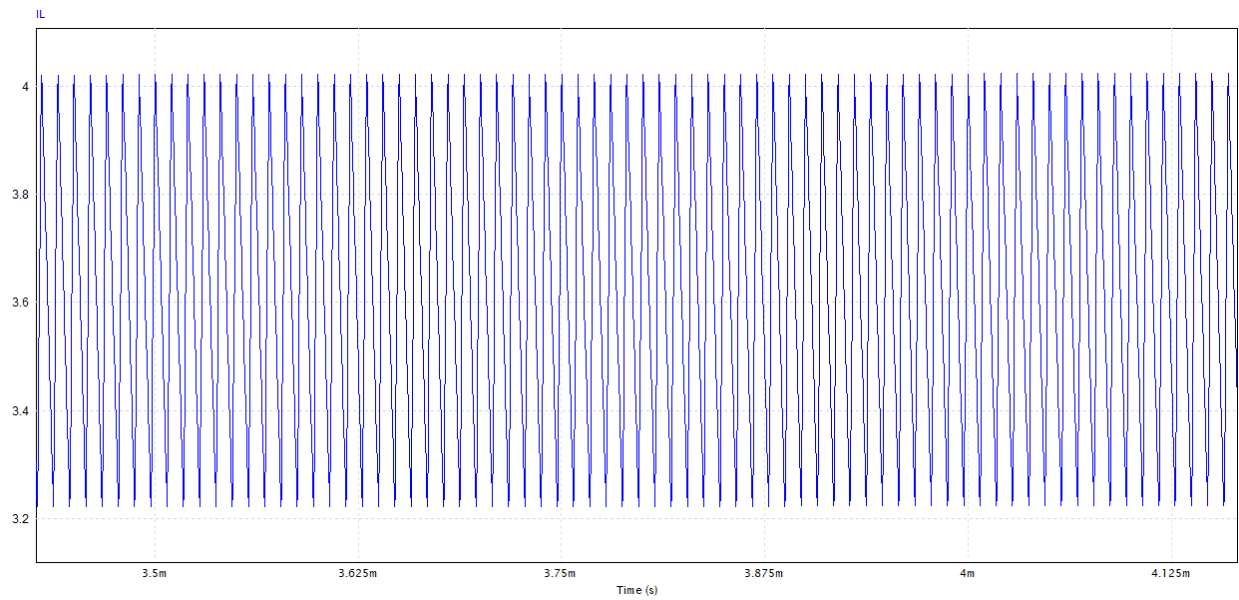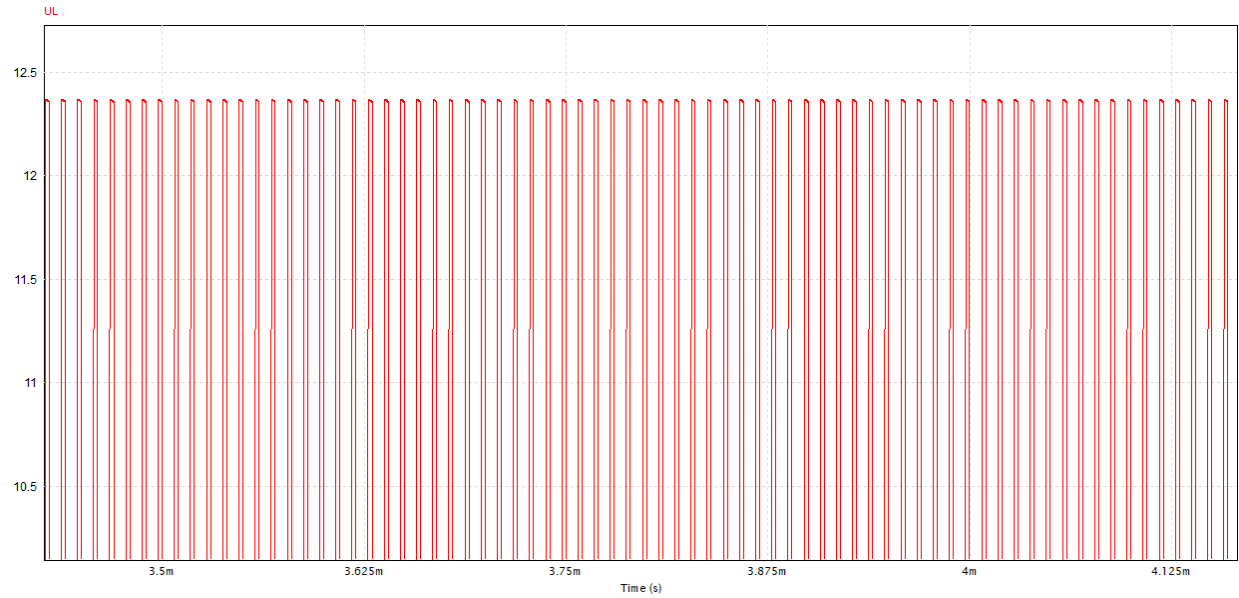

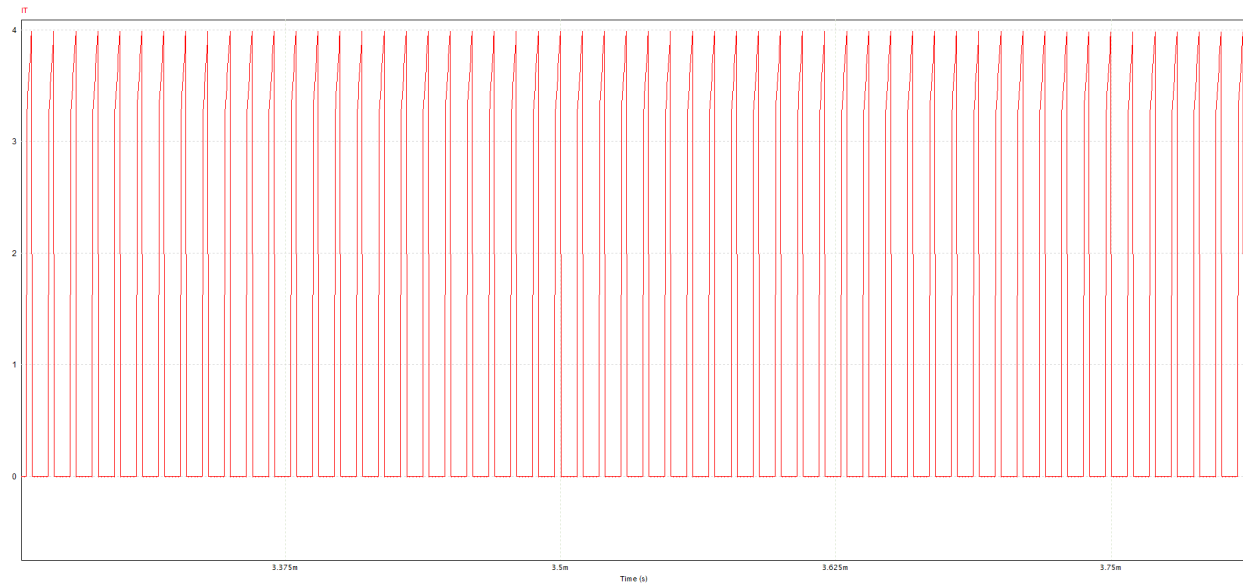

The PID controller

A PID controller is an instrument used in industrial control applications to regulate temperature, flow, pressure, speed and other process variables. PID (proportional integral derivative) controllers use a control loop feedback mechanism to control process variables and are the most accurate and stable controller.

Calculus (specifications taken from buck):

$$\begin{aligned}
 w0 &:= \frac{1}{\left(\sqrt{37.5 \mu\text{H} \cdot 200 \mu\text{F}}\right)} = 11.547 \text{ kHz} \\
 w_{fz} &:= w0 & w_{hf} &:= 314 \text{ kHz} \\
 w_{zea} &:= w_{fz} \\
 R_{fbt} &:= 25 \text{ k}\Omega & w_{fp} &:= \frac{1}{(0.01 \Omega \cdot 200 \mu\text{F})} = 500 \text{ kHz} \\
 R_{comp} &:= 8.742 \cdot R_{fbt} = 218.55 \text{ k}\Omega \\
 C_{ff} &:= \frac{1}{w_{fz} \cdot R_{fbt}} = 3.464 \text{ nF} \\
 C_{comp} &:= \frac{1}{(w_{zea} \cdot R_{comp})} = 0.396 \text{ nF} \\
 C_{hf} &:= \frac{1}{(w_{hf} \cdot R_{comp})} = 0.015 \text{ nF} \\
 R_{ff} &:= \frac{1}{(w_{fp} \cdot C_{ff})} = 577.35 \Omega \\
 R_{fbb} &:= \frac{(R_{fbt} \cdot 4)}{4 - 2.5} = 66.667 \text{ k}\Omega
 \end{aligned}$$

Simulations:

